



浙江大学
ZHEJIANG UNIVERSITY

Logic and Computer Design Fundamentals

Chapter 2 –Combinational Logic Circuits(1)


Ma De (马德)

made@zju.edu.cn

2023

College of Computer Science, Zhejiang University

Course Outline

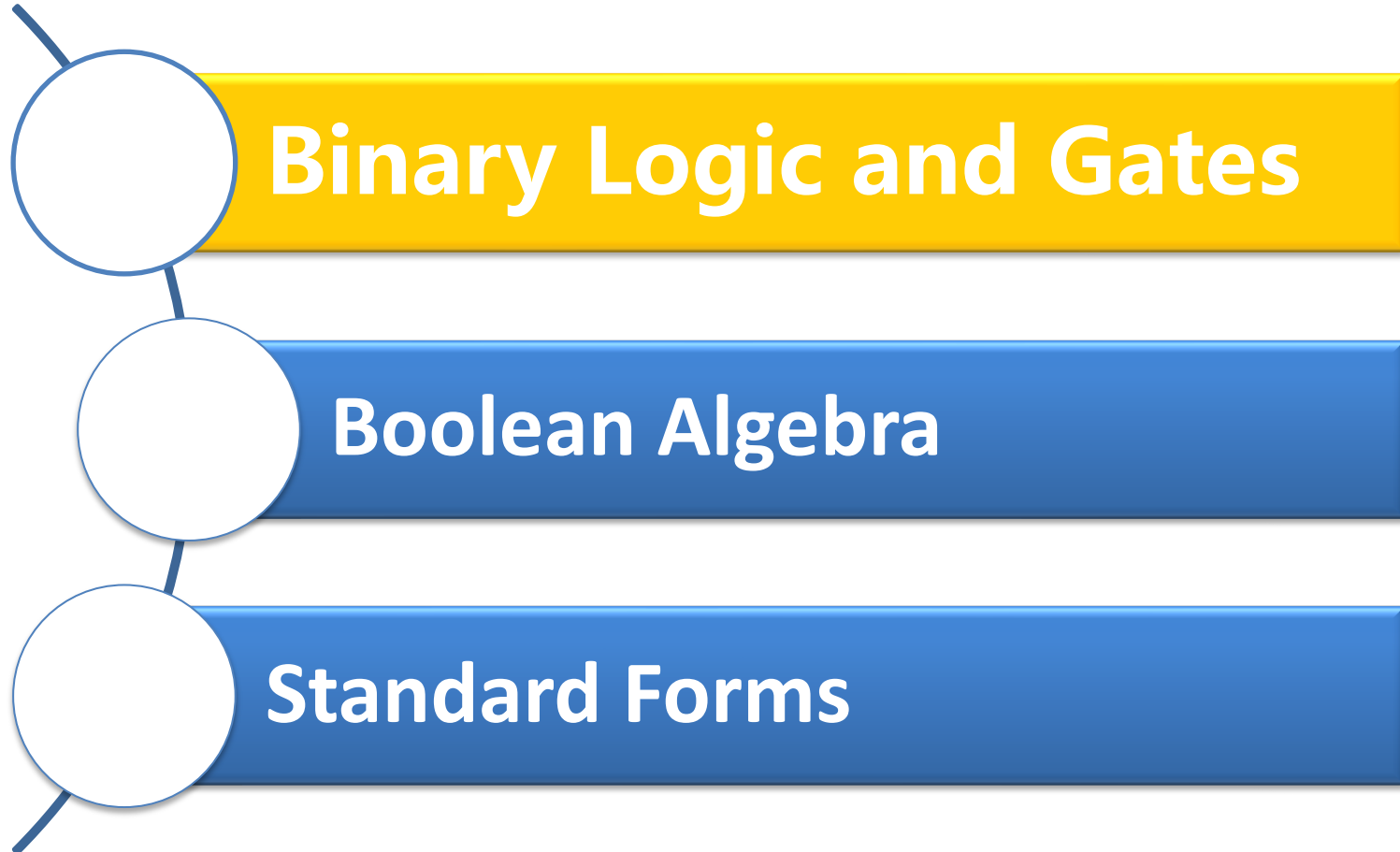

Binary Logic and Gates

□ Binary Logic

■ Binary variables

- take on one of two values, 1 and 0
 - A, B, y, z, or X_1 for now, RESET, START_IT, or ADD1 later

■ Logical operators

- operate on binary values and binary variables.
- Basic logical operators are the logic functions AND, OR and NOT.

□ Logic gates

- implement logic functions.
- Basic circuits

□ Boolean Algebra

- a useful mathematical system for specifying and transforming logic functions.
- We study Boolean algebra as a foundation for designing and analyzing digital systems!

Logical Operations

- The three basic logical operations are:
 - AND
 - OR
 - NOT
- AND is denoted by a dot ($\cdot$), $\times$, $\wedge$, or even none.
- OR is denoted by a plus ($+$) or $\vee$, $.$
- NOT is denoted by an overbar ($\bar{}$), a single quote mark ($'$) after, or ($\sim$) before the variable.



Logical Operations

□ **AND:** is read “Z is equal to X AND Y.”

Z = 1 if and only if X = 1 and Y = 1; otherwise Z = 0;

□ **OR:** is read “Z is equal to X OR Y.”

Z = 1 if X = 1 or if Y = 1, or if both X = 1 and Y = 1;
Z = 0 if and only if X = 0 and Y = 0;

□ **NOT:** is read “Z is equal to NOT X.”

If X = 1, Z = 0; but if X = 0, then Z = 1

Operator Definitions

- Operations are defined on the values "0" and "1" for each operator:

AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

NOT

$$\overline{0} = 1$$

$$\overline{1} = 0$$

- Note: The statement:**

- $1 + 1 = 2$ (read “one plus one equals two”)

is not the same as

- $1 + 1 = 1$ (read “1 or 1 equals 1”).

Truth Tables

- **Truth table** – a tabular listing of the values of a function for all possible combinations of values on its arguments
- **Example: Truth tables for the basic logic operations:**

AND		
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT	
X	$Z = \bar{X}$
0	1
1	0

Logic Function Implementation

□ Using Switches

■ For inputs:

- logic 1 is switch closed
- logic 0 is switch open


■ For outputs:

- logic 1 is light on
- logic 0 is light off.


■ NOT uses a switch such that:

- logic 1 is switch open
- logic 0 is switch closed


Switches in parallel $\Rightarrow$ OR

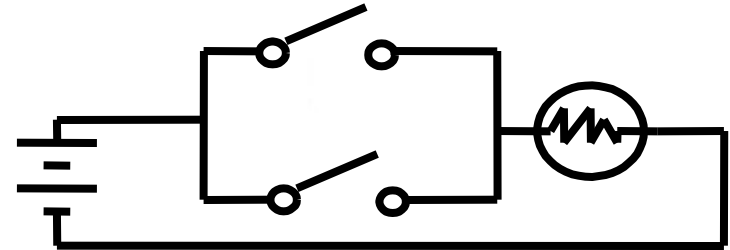

Switches in series $\Rightarrow$ AND

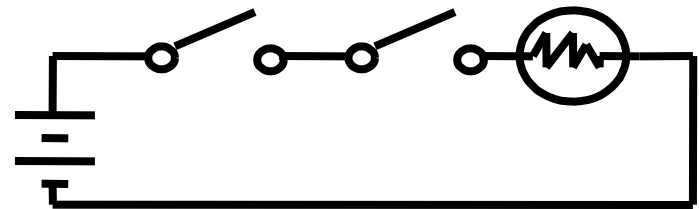


Normally-closed switch $\Rightarrow$ NOT

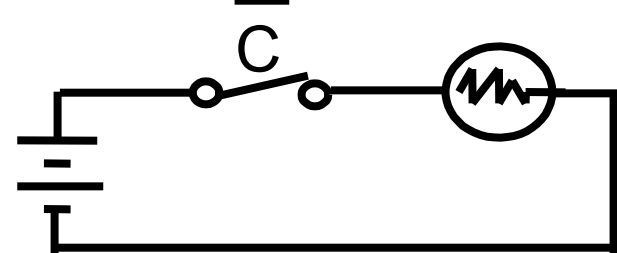

Logic Function Implementation (Continued)



□ Example: Logic Using Switches

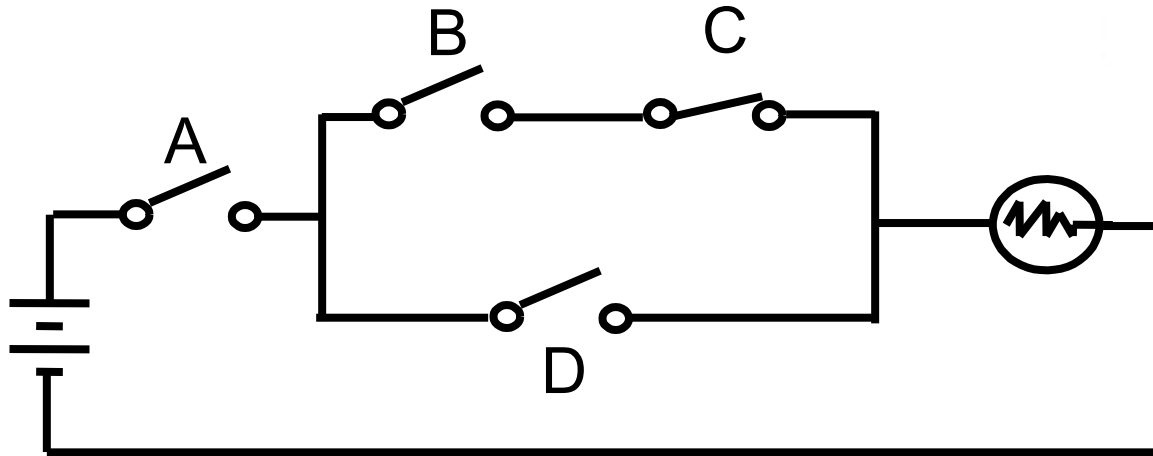

□ Light is on ($L = 1$) for

$$L(A, B, C, D) = A((B C) + D) = A B C + A D$$




and off ($L = 0$), otherwise.

Logic Gates

- ❑ In the earliest computers, switches were opened and closed by magnetic fields produced by energizing coils in *relays*. The switches in turn opened and closed the current paths.
- ❑ Later, *vacuum tubes* that open and close current paths electronically replaced relays.
- ❑ Today, *transistors* are used as electronic switches that open and close current paths.


Logic Gate Symbols and Behavior

□ Logic gates have special symbols:

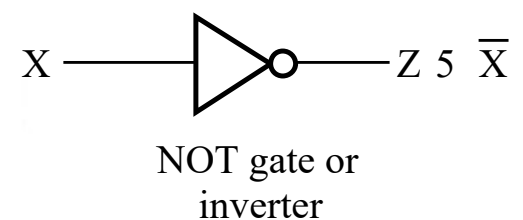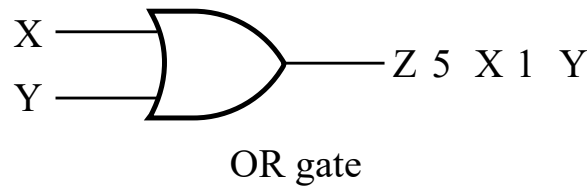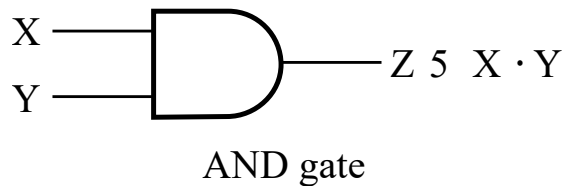

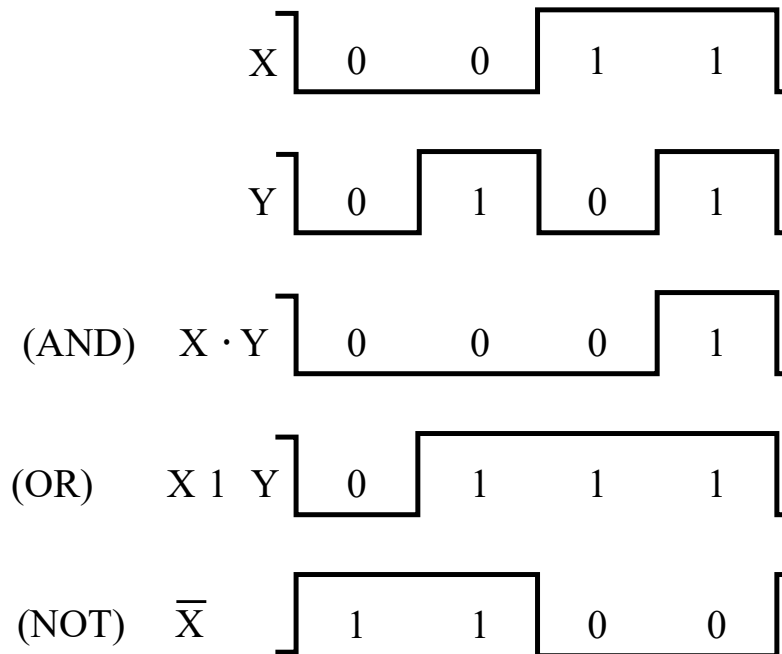(a) Graphic symbols


□ And waveform behavior in time as follows:



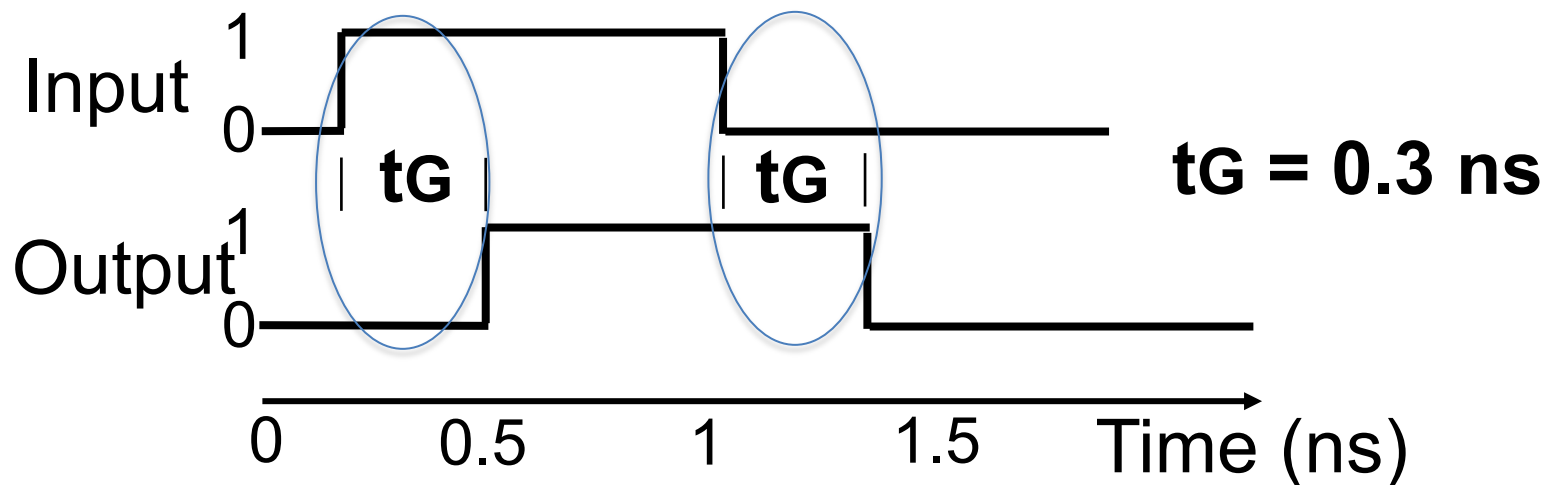(b) Timing diagram

Gate Delay

- ❑ In actual physical gates, if one or more input changes causes the output to change, the output change does not occur instantaneously.
- ❑ The delay between an input change(s) and the resulting output change is the *gate delay* denoted by t_G :





NOT AND (NAND)

True and False

A	B	L
F	F	T
T	F	T
F	T	T
T	T	F

1 and 0

A	B	L
0	0	1
1	0	1
0	1	1
1	1	0

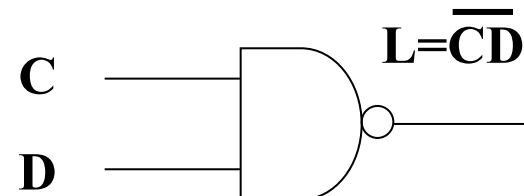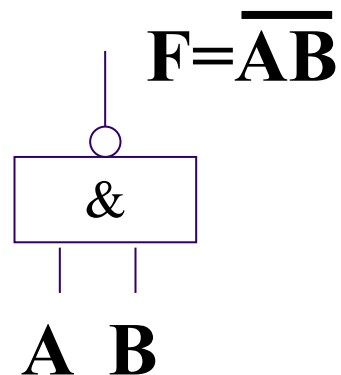


Graphic symbols

NOT OR (NOR)


True and False

A	B	L
F	F	T
T	F	F
F	T	F
T	T	F

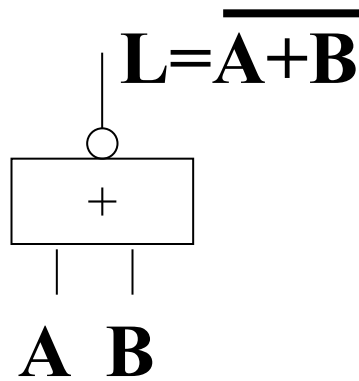

1 and 0


A	B	L
0	0	1
1	0	0
0	1	0
1	1	0

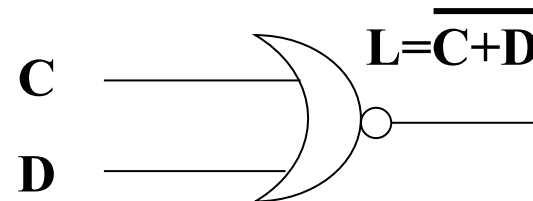

Graphic symbols

AND-OR-INVERT (AOI)

0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

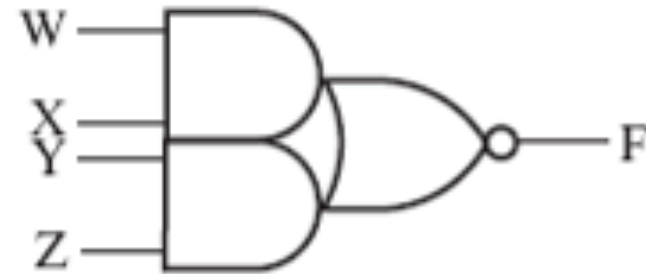

Graphic symbols



Exclusive-OR (XOR)

True and False

<i>A</i>	<i>B</i>	<i>L</i>
F	F	F
T	F	T
F	T	T
T	T	F

1 and 0

<i>A</i>	<i>B</i>	<i>L</i>
0	0	0
1	0	1
0	1	1
1	1	0

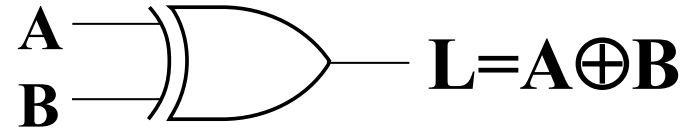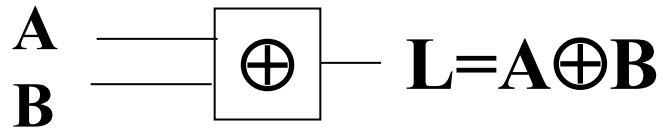

Graphic symbols



Eight Identities of XOR

$$X \oplus 0 = X$$

$$X \oplus 1 = \overline{X}$$

$$X \oplus X = 0$$

$$X \oplus \overline{X} = 1$$

$$X \oplus \overline{Y} = \overline{X \oplus Y}$$

$$\overline{X} \oplus Y = \overline{X \oplus Y}$$

$$X \oplus Y = Y \oplus X$$

$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z$$

$$X \oplus Y = X\overline{Y} + \overline{X}Y$$




Exclusive-NOR (XNOR)

True and False

A	B	L
F	F	T
T	F	F
F	T	F
T	T	T

1 and 0


A	B	L
0	0	1
1	0	0
0	1	0
1	1	1

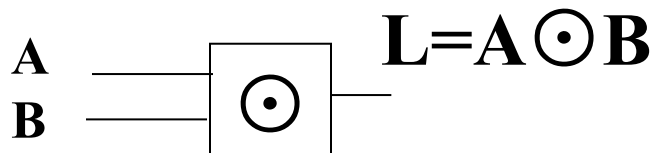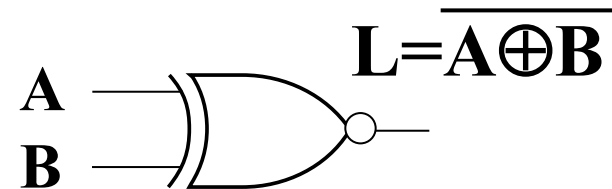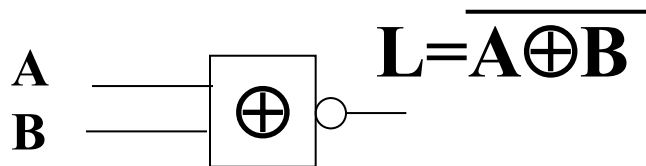


Graphic symbols

Multiple-input gates

OR:

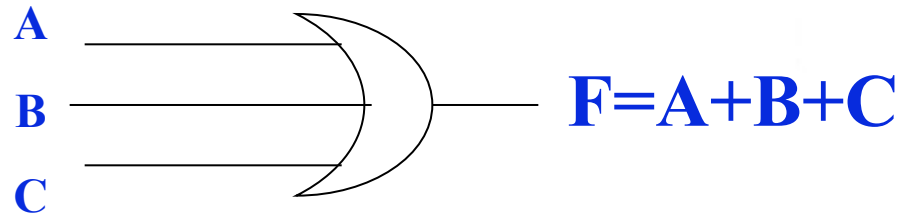


AND:

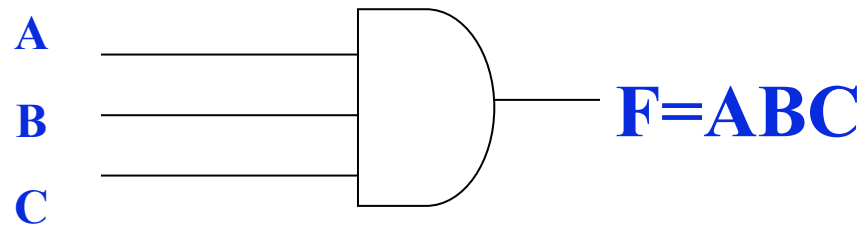

HDL-Verilog example

Truth Table for the Function $L = D\bar{X} + A$


D	X	A	L
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

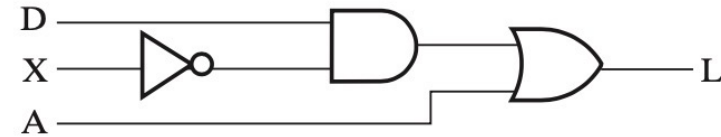


```

module fig2_5 (L, D, X, A);
    input D, X, A;
    output L;
    wire X_n, t2;

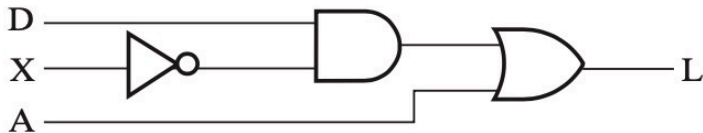    not (X_n, X);
    and (t2, D, X_n);
    or (L, t2, A);
endmodule
  
```



Course Outline

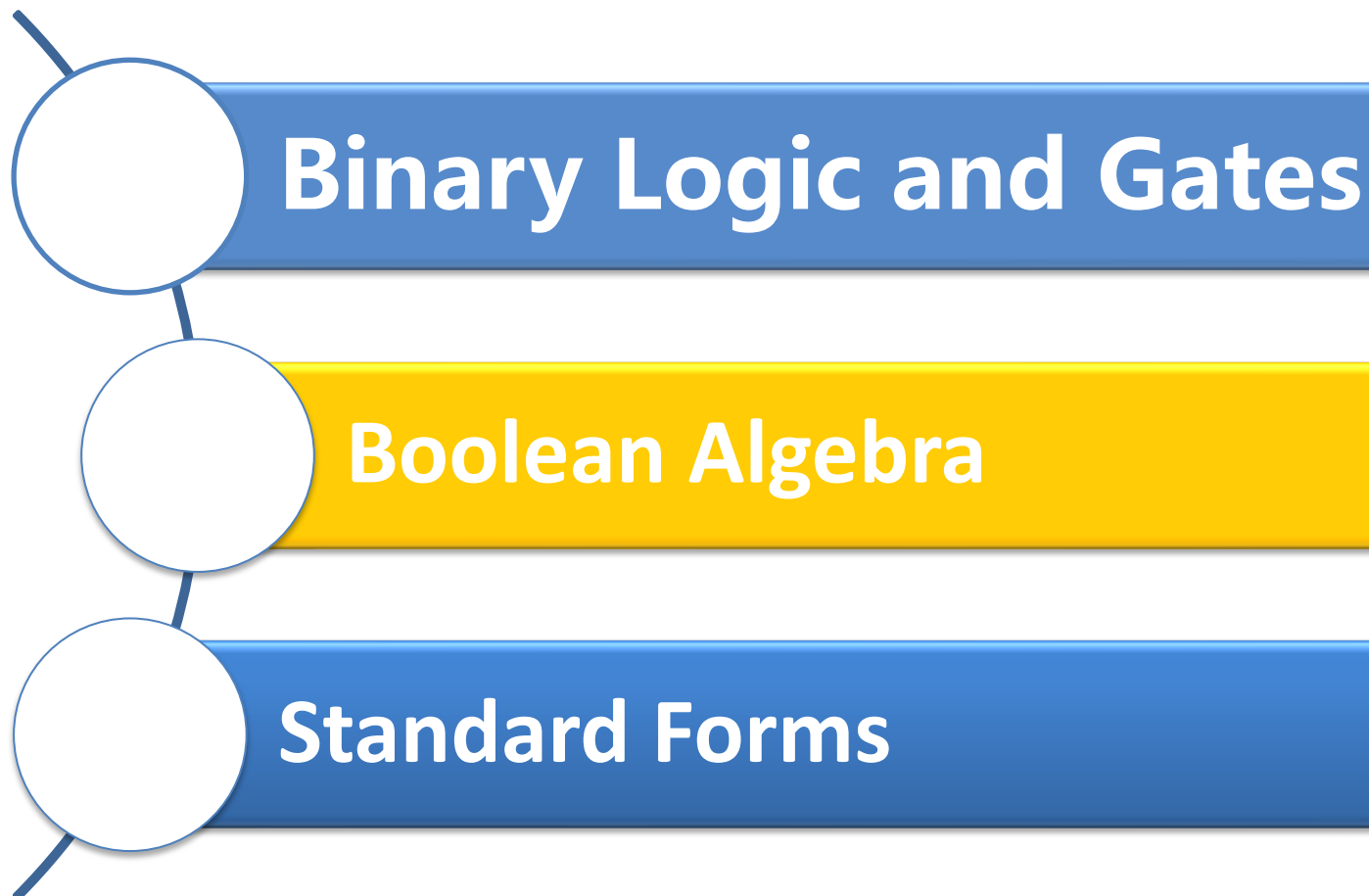

Basic concepts of Boolean algebra

□ Boolean Algebra:

- also called Logic Algebra , useful mathematical system for specifying and transforming logic functions.
- a foundation for designing and analyzing digital systems!

□ Logical variables

- Is a binary variable.
- Two logical values only take 0,1 (true, false).
- The logic value not size

□ Three basic functions:

- “AND” 、 “OR” 、 “NOT”

Boolean function defined

The definition of the logic function!!!

Assume a (circuit) input logic variable for $X_1, X_2, \dots, X_n$, and the output logic variable is F . When $X_1, X_2, \dots, X_n$ value is determined, the value of F is uniquely decided upon, then F is called to as $X_1, X_2, \dots, X_n$, the logic **function**, denoted as

$$F=f(X_1, X_2, \dots, X_n)$$

Note: Although $X+Y=X+Z$ or $XY=XZ$,

$Y = Z$ is impossible true

Boolean algebra representation

- Boolean algebra representation: The Expression constituted by the binary variables, constants 0 and 1, logical operators, and parentheses

For example: $F(X, Y, Z) = X + \bar{Y}Z$

- Function can be expressed in a variety of expressions , Function expressions isn't unique.
- A single output and multi-output
 - the latter require more than one function expression represents the output.

- Can also use a truth table

- A Boolean function is unique with a

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Basic Equation

□ Simplifying Boolean expressions with the properties

1.	$X + 0 = X$	2.	$X \cdot 1 = X$	
3.	$X + 1 = 1$	4.	$X \cdot 0 = 0$	
5.	$X + X = X$	6.	$X \cdot X = X$	
7.	$X + \bar{X} = 1$	8.	$X \cdot \bar{X} = 0$	
9.	$\bar{\bar{X}} = X$			
10.	$X + Y = Y + X$	11.	$XY = YX$	Commutative
12.	$(X + Y) + Z = X + (Y + Z)$	13.	$(XY)Z = X(YZ)$	Associative
14.	$X(Y + Z) = XY + XZ$	15.	$X + YZ = (X + Y)(X + Z)$	Distributive
16.	$\overline{X + Y} = \bar{X} \cdot \bar{Y}$	17.	$\overline{X \cdot Y} = \bar{X} + \bar{Y}$	DeMorgan's

Boolean function equal

□ Assuming two logical function

$$F_1 = f_1(X_1, X_2, \dots, X_n)$$

$$F_2 = f_2(X_1, X_2, \dots, X_n)$$

If corresponding to $X_1, X_2, \dots, X_n$ for **any set of values**, the value of F_1 and F_2 are **the same**, then the functions F_1 is equal to the function F_2 .

$$\text{记作: } F_1 = F_2$$

Truth table is completely identical!!!



Complementing and Duality rules

Complementing function

反函数

AND、OR swap, 0、1 swap
& Put variable Inverses

For logic function F , interchange **AND** and **OR** operators ; complement each **constant value** and **literal**, then obtained the new function is the inverse function of the original function is referred to as: $\overline{F}$

For example : known $F = \overline{A}B + C\overline{D}$

According to inversion Rules can be obtained :

$$\overline{F} = (A + \overline{B}) \cdot (\overline{C} + D)$$

Note the following two points:

- ① The holding operation **priority** unchanged, if necessary, add brackets indicate.
- ② Within converting, **public non-operation** remains unchanged for several variables

For example 1: $F = \overline{A} + \overline{B} \cdot (C + \overline{D}E)$, 则

$$\overline{F} = A \cdot [B + \overline{C}(D + \overline{E})]$$
$$\overline{F} \neq A \cdot B + \overline{C} \cdot D + \overline{E}$$

Example 2:

$$L = A \cdot B + C + \overline{\overline{D}}$$
$$\overline{L} = \overline{A} + \overline{\overline{B} \cdot \overline{C} \cdot D}$$

Duality rules

AND、OR swap, 0、1 swap
对偶规则 let variable unchanged



For logic function F , all “**AND**” changed to “**OR**”、
“**OR**” changed “**AND**”、 “**0**” changed to “**1**”、 “**1**” is
changed to “**0**”, then the resulting new logic function
 F' is F Duality function. **Variable don't Inverses!!!**

Seek a function F' Duality , the operation
sequence keep as same as the original function .

If F' is the F Duality, then F is also F' of Duality.
 F and F' is mutually Duality formula .

If the two logical functions **F and G** are **equal**, then the
Duality formula **F' and G'** are also **equal**.



Property of **Duality** of Boolean algebra

- Unless it happens to be self-dual, the dual of an expression does not equal the expression itself.
- Self-dual

Example: $H = A \cdot B + A \cdot C + B \cdot C$

$$\text{dual } H = (A + B)(A + C)(B + C)$$

$$= (A + BC)(B + C) = AB + AC + BC.$$

So H is self-dual !



Other Useful Theorems

$$x \times y + \bar{x} \times y = y \quad (x + y)(\bar{x} + y) = y \quad \text{Minimization}$$

$$x + x \cdot y = x \quad x \cdot (x + y) = x \quad \text{Absorption}$$

$$x + \bar{x} \times y = x + y \quad x \times (\bar{x} + y) = x \times y \quad \text{Simplification}$$

$$x \times y + \bar{x} \times z + y \times z = x \times y + \bar{x} \times z$$

$$(x + y) \times (\bar{x} + z) \times (y + z) = (x + y) \times (\bar{x} + z) \quad \text{Consensus}$$

$$\overline{x + y} = \bar{x} \times \bar{y} \quad \overline{x \times y} = \bar{x} + \bar{y} \quad \text{DeMorgan's Laws}$$

Proof of Absorption Theorem

□ $A + A \cdot B = A$

(Absorption Theorem)

Proof Steps

Justification (identity or theorem)

$$A + A \cdot B$$

$$= A \cdot 1 + A \cdot B$$

$$X = X \cdot 1$$

$$= A \cdot (1 + B)$$

$$X \cdot Y + X \cdot Z = X \cdot (Y + Z) \text{ (Distributive Law)}$$

$$= A \cdot 1$$

$$1 + X = 1$$

$$= A$$

$$X \cdot 1 = X$$

□ Compute the dual on both sides, the equation is equal either

$$A \cdot (A+B) = A$$



Proof of Minimization Theorem

Proof Steps	Justification (identity or theorem)
$AB + A\bar{B}$	
$= A(B + \bar{B})$	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$ (Distributive Law)
$= A \cdot 1$	$1 + X = 1$
$= A$	

- Compute the dual on both sides, the equation is equal either

$$(A+B) \cdot (A+\bar{B}) = A$$

Proof of Simplification Theorem

□ $A + \overline{AB} = A + B$ (Simplification Theorem)

Proof Steps

Justification (identity or theorem)

$$\begin{aligned} & A + \overline{AB} \\ = & (A + \overline{A})(A + B) & X + Y \cdot Z = (X + Y) \cdot (X + Z) \text{ (Distributive Law)} \end{aligned}$$

$$= 1 \cdot (A + B)$$

$$X + \overline{X} = 1$$

$$= A + B$$

□ Compute the dual on both sides, the equation is equal either

$$\overline{A(\overline{A+B})} = \overline{AB}$$

Proof of Consensus Theorem

□ $AB + \overline{A}C + BC = AB + \overline{A}C$ (Consensus Theorem)

Proof Steps

Justification (identity or theorem)

$$\begin{aligned} & AB + \overline{A}C + BC \\ = & AB + \overline{A}C + 1 \cdot BC & ? \\ = & AB + \overline{A}C + (A + \overline{A}) \cdot BC & ? \end{aligned}$$

$$\begin{aligned} & AB + A'C + ABC + A'BC \\ = & AB + ABC + A'C + A'BC \\ = & AB \cdot 1 + ABC + A'C \cdot 1 + A'C \cdot B \end{aligned}$$

$$\begin{aligned} = & AB(1 + C) + A'C(1 + B) \\ = & AB \cdot 1 + A'C \cdot 1 = AB + A'C \end{aligned}$$

$$X(Y + Z) = XY + XZ \text{ (Distributive Law)}$$

$$X + Y = Y + X \text{ (Commutative Law)}$$

$$X \cdot 1 = X, X \cdot Y = Y \cdot X \text{ (Commutative Law)}$$

$$X(Y + Z) = XY + XZ \text{ (Distributive Law)}$$

$$X \cdot 1 = X$$

Proof of the 15th basic identity

□ Using the absorption theorem

$$X + XY = X$$

□ $X + YZ = (X+Y)(X+Z)$

■ From the right side

$$\begin{aligned}(X+Y)(X+Z) &= X+XY+XZ+YZ \\ &= X + XZ + YZ \\ &= X + YZ\end{aligned}$$

Example: Boolean Algebraic Proof



$$(\overline{X + Y})Z + X\overline{Y} = \overline{Y}(X + Z)$$

Proof Steps

Justification (identity or theorem)

$$(\overline{X + Y})Z + X\overline{Y}$$

$$\begin{aligned} & X'Y'Z + XY' \\ &= Y'X'Z + Y'X \\ &= Y'(X'Z + X) \\ &= Y'(X' + X)(Z + X) \\ &= Y' \cdot 1 \cdot (Z + X) \\ &= Y'(X + Z) \end{aligned}$$

$$\begin{aligned} & (A + B)' = A' \cdot B' \text{ (DeMorgan's Law)} \\ & A \cdot B = B \cdot A \text{ (Commutative Law)} \\ & A(B + C) = AB + AC \text{ (Distributive Law)} \\ & A + BC = (A + B)(A + C) \text{ (Distributive Law)} \\ & A + A' = 1 \\ & 1 \cdot A = A, A + B = B + A \text{ (Commutative Law)} \end{aligned}$$



Any logical equation that contains a variable A , and if all occurrences of A 's position are replaced with a logical function F , the equation still holds .

Example

Assume: $X(Y+Z)=XY+XZ$, if $X + YZ$

Instead of X , then equation still holds :

$$(X+YZ) (Y+Z)=(X+YZ)Y+(X+YZ)Z$$

■ Similarly equation (complementary)

$$f(X_1, X_2, ..., X_n) + \overline{f}(X_1, X_2, ..., X_n) = 1$$

Additional equation

□ Equation 1:

Shannon formula

- Assuming: Function F contained variables x 、 $\bar{x}$, at " x AND F" operation, variable x may be replaced by "1", variable $\bar{x}$ can be replaced by "0". at " $\bar{x}$ AND F" operation, x can be "0", $\bar{x}$ can be replaced with "1".

$$x f(x, \bar{x}, y, \dots, z_n) = x f(1, 0, y, \dots, z)$$

$$\bar{x} f(x, \bar{x}, y, \dots, z_n) = \bar{x} f(0, 1, y, \dots, z)$$

- This expression is actually expansion:

$$X \cdot \bar{X} = 0 \text{ and } X \cdot X = X$$

Similarly, based on $A + \bar{A} = 1$, $A + \bar{A}B = A + B$, and $A + AB = A$, we can obtain the following equation

$$x + f(x, \bar{x}, y, \dots, z) = x + f(0, 1, y, \dots, z)$$

$$\bar{x} + f(x, \bar{x}, y, \dots, z) = \bar{x} + f(1, 0, y, \dots, z)$$

Additional equation is very useful for simplifying.

Example : $f = xy + x\bar{z} + (\bar{x} + \bar{y})(x + z)$, 求 $x \cdot f$

$$\begin{aligned} x \cdot f &= x[xy + x\bar{z} + (\bar{x} + \bar{y})(x + z)] \\ &= x[1 \cdot y + 0 \cdot z + (0 + \bar{y})(1 + z)] \\ &= x(y + \bar{y}) = x \end{aligned}$$

◆ **Equation 2:** The function F contains the both of the variables x 、 $\bar{x}$, may be follow:

$$\begin{aligned} F(X, \bar{X}, Y \dots Z) &= x \cdot f(x, \bar{x}, y, \dots z) + \bar{x} f(x, \bar{x}, y, \dots z) \\ &= x f(1, 0, y, \dots z) + \bar{x} f(0, 1, y, \dots z) \end{aligned}$$

逻辑函数分解

(Problem 3-2)

◆ The same duality formula:

$$F(x, \bar{x}, y, \dots z) = [x + f(1, 0, y, \dots z)] \cdot [\bar{x} + f(0, 1, y, \dots z)]$$

Shannon expansion

Equation 1 and Equation 2 can be obtained::

$$\begin{aligned} f(x_1, x_2, x_3) &= x_1 x_2 x_3 f(1, 1, 1) + x_1 x_2 \bar{x}_3 f(1, 1, 0) \\ &\quad + x_1 \bar{x}_2 x_3 f(1, 0, 1) + x_1 \bar{x}_2 \bar{x}_3 f(1, 0, 0) \\ &\quad + \bar{x}_1 x_2 x_3 f(0, 1, 1) + \bar{x}_1 x_2 \bar{x}_3 f(0, 1, 0) \\ &\quad + \bar{x}_1 \bar{x}_2 x_3 f(0, 0, 1) + \bar{x}_1 \bar{x}_2 \bar{x}_3 f(0, 0, 0) \end{aligned}$$

Expression Simplification

- Target: the smallest number of literals and the smallest number of terms (complemented and uncomplemented variables):
- AND-OR forms

$$\begin{aligned} & A B + \bar{A} C D + \bar{A} B D + \bar{A} C \bar{D} + A B C D \\ &= A B + A B C D + \bar{A} C D + \bar{A} C \bar{D} + \bar{A} B D \\ &= A B + A B (C D) + \bar{A} C (D + \bar{D}) + \bar{A} B D \\ &= A B + \bar{A} C + \bar{A} B D = B (A + \bar{A} D) + \bar{A} C \\ &= B (A + D) + \bar{A} C \quad 5 \text{ literals} \end{aligned}$$

Expression Simplification

□ OR-AND forms

$$F = (\bar{A} + \bar{B})(\bar{A} + \bar{C} + D)(A + C)(B + \bar{C})$$


□ Dual

$$\begin{aligned} F' &= \bar{A}\bar{B} + \bar{A}\bar{C}D + AC + B\bar{C} \\ &= (\bar{A}\bar{B} + B\bar{C} + \bar{A}\bar{C}D) + AC \\ &= \bar{A}\bar{B} + B\bar{C} + AC \end{aligned}$$

□ Dual of $F' \Rightarrow F$

$$F = F'' = (\bar{A} + \bar{B})(B + \bar{C})(A + C)$$

Course Outline

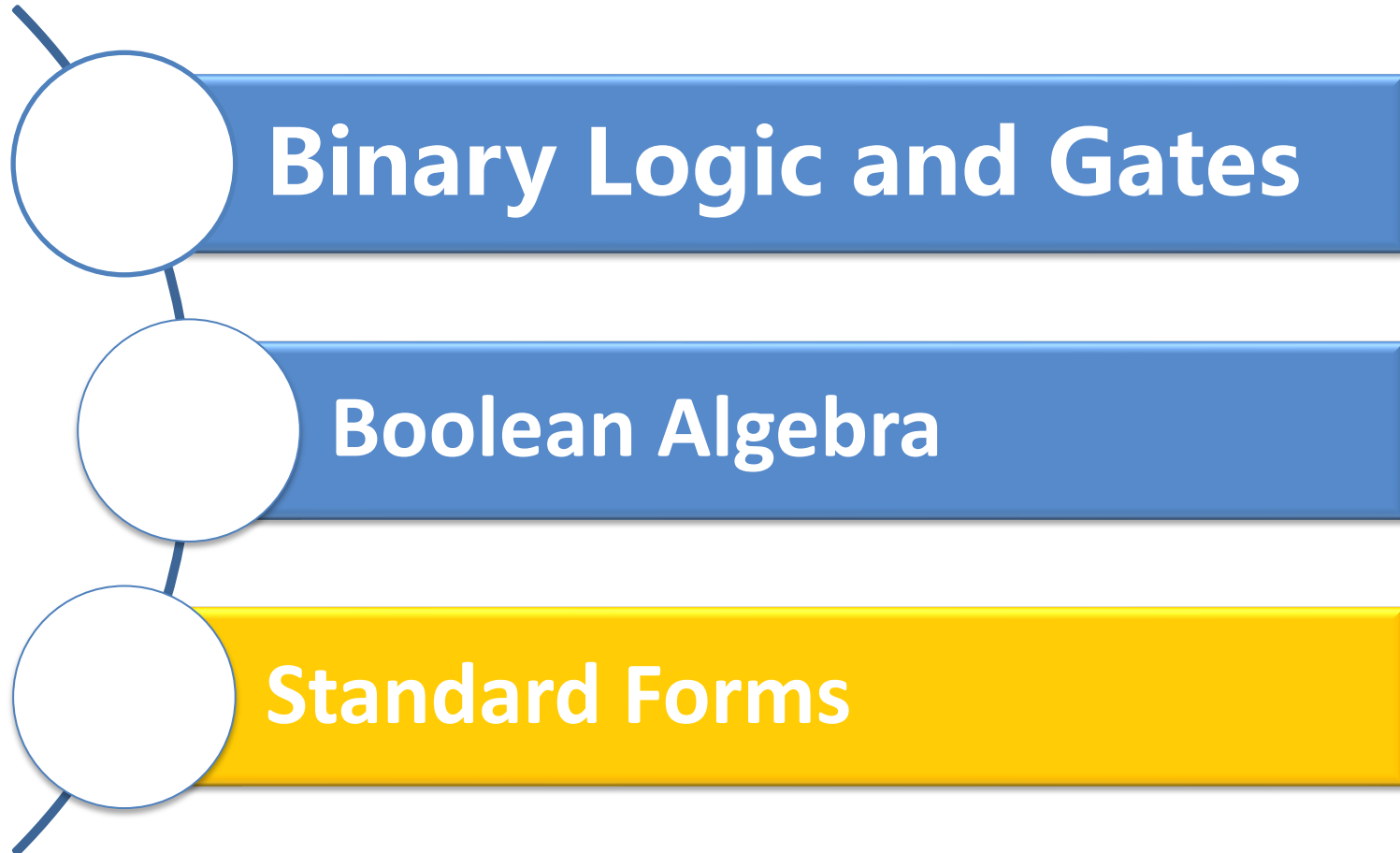



Overview – Canonical Forms

- ❑ What are Canonical Forms?
- ❑ Minterms and Maxterms
- ❑ Index Representation of Minterms and Maxterms
- ❑ Sum-of-Minterm (SOM) Representations
- ❑ Product-of-Maxterm (POM) Representations
- ❑ Representation of Complements of Functions
- ❑ Conversions between Representations

Canonical Forms

- ❑ It is useful to specify Boolean functions in a form that:
 - Allows comparison for equality.
 - Has a correspondence to the truth tables
- ❑ Canonical Forms in common usage:
 - Sum of Minterms (SOM)
 - Product of Maxterms (POM)
 - Any function can be expressed to the canonical form

Minterms

- Minterms are AND terms with every variable present in either true or complemented form.
- Given that each binary variable may appear normal (e.g. x) or complemented (e.g. x'), there are 2^n minterms for n variables.

X	Y	Z	Product Term	Symbol	m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7
0	0	0	$\overline{X}\overline{Y}\overline{Z}$	m_0	1	0	0	0	0	0	0	0
0	0	1	$\overline{X}\overline{Y}Z$	m_1	0	1	0	0	0	0	0	0
0	1	0	$\overline{X}Y\overline{Z}$	m_2	0	0	1	0	0	0	0	0
0	1	1	$\overline{X}YZ$	m_3	0	0	0	1	0	0	0	0
1	0	0	$X\overline{Y}\overline{Z}$	m_4	0	0	0	0	1	0	0	0
1	0	1	$X\overline{Y}Z$	m_5	0	0	0	0	0	1	0	0
1	1	0	$XY\overline{Z}$	m_6	0	0	0	0	0	0	1	0
1	1	1	XYZ	m_7	0	0	0	0	0	0	0	1

Minterms

- ❑ **Complemented or uncomplemented? A literal is**
 - complemented if the corresponding bit is 0
 - Uncomplemented if the corresponding bit is 1
- ❑ **The index: the decimal equivalent of the binary combination corresponding to the Minterm**

X	Y	Z	Product Term	Symbol	m ₀	m ₁	m ₂	m ₃	m ₄	m ₅	m ₆	m ₇
0	0	0	$\bar{X}\bar{Y}\bar{Z}$	m ₀	1	0	0	0	0	0	0	0
0	0	1	$\bar{X}\bar{Y}Z$	m ₁	0	1	0	0	0	0	0	0
0	1	0	$\bar{X}Y\bar{Z}$	m ₂	0	0	1	0	0	0	0	0
0	1	1	$\bar{X}YZ$	m ₃	0	0	0	1	0	0	0	0
1	0	0	$X\bar{Y}\bar{Z}$	m ₄	0	0	0	0	1	0	0	0
1	0	1	$X\bar{Y}Z$	m ₅	0	0	0	0	0	1	0	0
1	1	0	$XY\bar{Z}$	m ₆	0	0	0	0	0	0	1	0
1	1	1	XYZ	m ₇	0	0	0	0	0	0	0	1

Maxterms

- Maxterms are OR terms with every variable in true or complemented form.
- Given that each binary variable may appear normal (e.g., x) or complemented (e.g., x'), there are 2^n maxterms for n variables.

X	Y	Z	Sum Term	Symbol	M_0	M_1	M_2	M_3	M_4	M_5	M_6	M_7
0	0	0	$X+Y+Z$	M_0	0	1	1	1	1	1	1	1
0	0	1	$X+Y+\bar{Z}$	M_1	1	0	1	1	1	1	1	1
0	1	0	$X+\bar{Y}+Z$	M_2	1	1	0	1	1	1	1	1
0	1	1	$X+\bar{Y}+\bar{Z}$	M_3	1	1	1	0	1	1	1	1
1	0	0	$\bar{X}+Y+Z$	M_4	1	1	1	1	0	1	1	1
1	0	1	$\bar{X}+Y+\bar{Z}$	M_5	1	1	1	1	1	0	1	1
1	1	0	$\bar{X}+\bar{Y}+Z$	M_6	1	1	1	1	1	1	0	1
1	1	1	$\bar{X}+\bar{Y}+\bar{Z}$	M_7	1	1	1	1	1	1	1	0

Maxterms

- **Complemented or uncomplemented? A literal is**
 - complemented if the corresponding bit is **1**
 - Uncomplemented if the corresponding bit is **0**
- **The index: the decimal equivalent of the binary combination corresponding to the Maxterm**

X	Y	Z	Sum Term	Symbol	M ₀	M ₁	M ₂	M ₃	M ₄	M ₅	M ₆	M ₇
0	0	0	$X+Y+Z$	M ₀	0	1	1	1	1	1	1	1
0	0	1	$X+Y+\bar{Z}$	M ₁	1	0	1	1	1	1	1	1
0	1	0	$X+\bar{Y}+Z$	M ₂	1	1	0	1	1	1	1	1
0	1	1	$X+\bar{Y}+\bar{Z}$	M ₃	1	1	1	0	1	1	1	1
1	0	0	$\bar{X}+Y+Z$	M ₄	1	1	1	1	0	1	1	1
1	0	1	$\bar{X}+Y+\bar{Z}$	M ₅	1	1	1	1	1	0	1	1
1	1	0	$\bar{X}+\bar{Y}+Z$	M ₆	1	1	1	1	1	1	0	1
1	1	1	$\bar{X}+\bar{Y}+\bar{Z}$	M ₇	1	1	1	1	1	1	1	0

Minterm and Maxterm Relationship

□ Review: DeMorgan's Theorem

$$\overline{x \cdot y} = \bar{x} + \bar{y} \quad \text{and} \quad \overline{x + y} = \bar{x} \times \bar{y}$$

□ Two-variable example:

$$M_2 = \bar{x} + y \quad \text{and} \quad \bar{m}_2 = x \cdot \bar{y}$$

Thus M_2 is the complement of m_2 and vice-versa.

□ Since DeMorgan's Theorem holds for n variables, the above holds for terms of n variables

□ giving:

$$M_i = \bar{m}_i \quad \text{and} \quad m_i = \bar{M}_i$$

Thus M_i is the complement of m_i .

Index	Minterm	Maxterm
0	$\bar{x} \bar{y}$	$x + y$
1	$\bar{x} y$	$x + \bar{y}$
2	$x \bar{y}$	$\bar{x} + y$
3	$x y$	$\bar{x} + \bar{y}$

Observations

- ❑ In the function tables:
 - Each minterm has one and only one 1 present in the 2^n terms (a minimum of 1s). All other entries are 0.
 - Each maxterm has one and only one 0 present in the 2^n terms All other entries are 1 (a maximum of 1s).
- ❑ We can implement any function by "ORing" the minterms corresponding to "1" entries in the function table. These are called the minterms of the function.
- ❑ We can implement any function by "ANDing" the maxterms corresponding to "0" entries in the function table. These are called the maxterms of the function.
- ❑ This gives us two canonical forms:
 - Sum of Minterms (SOM)
 - Product of Maxterms (POM)for stating any Boolean function.

Sum of Minterms (SOM)

□ Example: Find $F_1 = m_1 + m_4 + m_7$

□ $F_1 = \bar{x} \bar{y} z + x \bar{y} \bar{z} + x y z$

x y z	index	m1 + m4 + m7 = F1					
0 0 0	0	0	+	0	+	0	= 0
0 0 1	1	1	+	0	+	0	= 1
0 1 0	2	0	+	0	+	0	= 0
0 1 1	3	0	+	0	+	0	= 0
1 0 0	4	0	+	1	+	0	= 1
1 0 1	5	0	+	0	+	0	= 0
1 1 0	6	0	+	0	+	0	= 0
1 1 1	7	0	+	0	+	1	= 1

Product of Maxterms (POM)

□ Example: Implement F1 in maxterms:

$$F_1 = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$$

$$F_1 = (x + y + z) \cdot (x + \bar{y} + z) \cdot (x + \bar{y} + \bar{z}) \cdot (\bar{x} + y + \bar{z}) \cdot (\bar{x} + \bar{y} + z)$$

x y z	i	$M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 = F_1$
0 0 0	0	$0 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 0$
0 0 1	1	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$
0 1 0	2	$1 \cdot 0 \cdot 1 \cdot 1 \cdot 1 = 0$
0 1 1	3	$1 \cdot 1 \cdot 0 \cdot 1 \cdot 1 = 0$
1 0 0	4	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$
1 0 1	5	$1 \cdot 1 \cdot 1 \cdot 0 \cdot 1 = 0$
1 1 0	6	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 0 = 0$
1 1 1	7	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$

Canonical Sum of Minterms

- Any Boolean function can be expressed as a Sum of Minterms.
 - For the function table, the minterms used are the terms corresponding to the 1's
 - For expressions, expand all terms first to explicitly list all minterms. Do this by “ANDing” any term missing a variable v with a term ($v + \bar{v}$).
- Example: Implement $f = x + \bar{x} \bar{y}$ as a sum of minterms.

First expand terms: $f = x(y + \bar{y}) + \bar{x} \bar{y}$

Then distribute terms: $f = \underline{xy} + x\bar{y} + \bar{x} \bar{y}$

Express as sum of minterms: $f = m_3 + m_2 + m_0 = \Sigma_m(0, 2, 3)$

Canonical Product of Maxterms


- Any Boolean Function can be expressed as a Product of Maxterms (POM).
 - For the function table, the maxterms used are the terms corresponding to the 0's.
 - For an expression, expand all terms first to explicitly list all maxterms. Do this by first applying the second distributive law, “ORing” terms missing variable v with a term equal to $v \times \bar{v}$ and then applying the distributive law again.
- Example: Convert to product of maxterms:

$$\begin{aligned} f(x, y, z) &= \bar{x} + \bar{x} \bar{y} \\ \text{Apply the distributive law:} \\ \bar{x} + \bar{x} \bar{y} &= (\bar{x} + \bar{x})(\bar{x} + \bar{y}) = 1 \times (\bar{x} + \bar{y}) = \bar{x} + \bar{y} \\ \text{Add missing variable } z: \\ \bar{x} + \bar{y} &= (\bar{x} + \bar{y} + z)(\bar{x} + \bar{y} + \bar{z}) \\ \text{Express as POM: } f &= M_2 \cdot M_3 = \prod_M(2, 3) \end{aligned}$$

Sum of Products, Products of Sum


□ Sum of products

$$F = \bar{Y} + \bar{X}Y\bar{Z} + XY$$

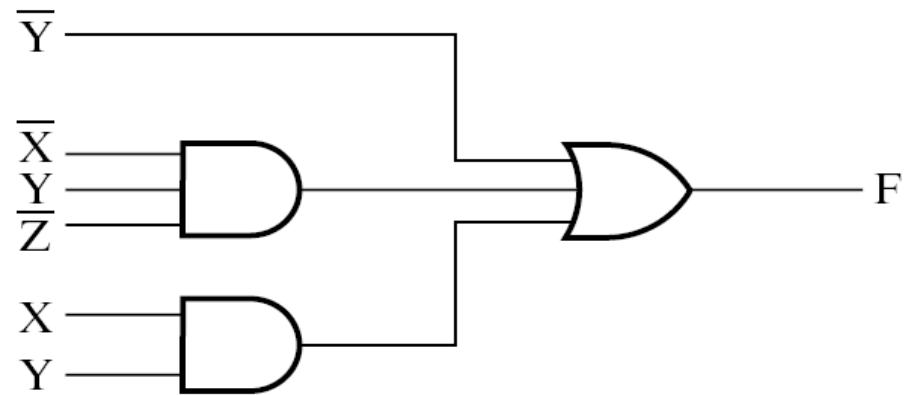

□ Product of sums

$$F = X(\bar{Y} + Z)(X + Y + \bar{Z})$$

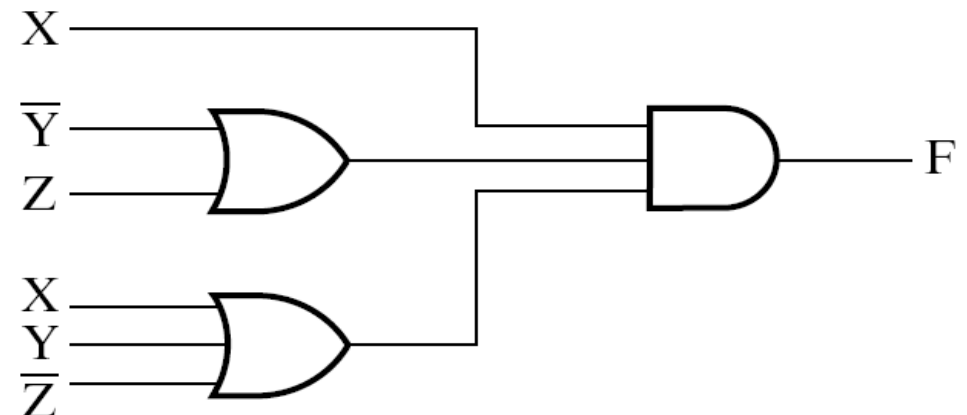

Function Complements

- ❑ The complement of a function expressed as a sum of minterms is constructed by selecting the minterms missing in the sum-of-minterms canonical forms.
- ❑ Alternatively, the complement of a function expressed by a Sum of Minterms form is simply the Product of Maxterms with the same indices.
- ❑ Example: Given $F(x, y, z) = \Sigma_m(1, 3, 5, 7)$

$$\bar{F}(x, y, z) = \Sigma_m(0, 2, 4, 6)$$

$$\bar{F}(x, y, z) = \Pi_M(1, 3, 5, 7)$$

Standard Forms

- Standard Sum-of-Products (SOP) form: equations are written as an OR of AND terms
- Standard Product-of-Sums (POS) form: equations are written as an AND of OR terms

- **Examples:**

- SOP: $\hat{A} B C + \bar{A} \bar{B} C + B$
- POS: $(A + B) \cdot (A + \bar{B} + \bar{C}) \cdot C$

- These “mixed” forms are neither SOP nor POS

- $(A B + C) (A + C)$
- $A B \bar{C} + A C (A + B)$

Standard Sum-of-Products (SOP)



- A sum of minterms form for n variables can be written down directly from a truth table.
 - Implementation of this form is a two-level network of gates such that:
 - The first level consists of n -input AND gates, and
 - The second level is a single OR gate (with fewer than 2^n inputs).
- This form often can be simplified so that the corresponding circuit is simpler.

Standard Sum-of-Products (SOP)

□ A Simplification Example:

$$F(A, B, C) = \Sigma m(1, 4, 5, 6, 7)$$

□ Writing the minterm expression:

$$F = \overline{A} \overline{B} C + \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C + \overline{A} B \overline{C} + A B C$$

□ Simplifying:

$$\begin{aligned} F &= A' B' C + A (B' C' + B C' + B' C + B C) \\ &= A' B' C + A (B' + B) (C' + C) \\ &= A' B' C + A \cdot 1 \cdot 1 \\ &= A' B' C + A \\ &= B' C + A \end{aligned}$$

□ Simplified F contains 3 literals compared with 15 in minterm F

SOP and POS Observations

- ❑ **The previous examples show that:**
 - **Canonical Forms (Sum-of-minterms, Product-of-Maxterms), or other standard forms (SOP, POS) differ in complexity**
 - **Boolean algebra can be used to manipulate equations into simpler forms.**
 - **Simpler equations lead to simpler two-level implementations**
- ❑ **Questions:**
 - **How can we attain a “simplest” expression?**
 - **Is there only one minimum cost circuit?**
 - **The next part will deal with these issues.**



Home Assignment

□ 2-1a; 2-2a, c; 2-3a, c; 2-6b, d; 2-10a, c; 2-11a, c, d; 2-12b; 2-15; 2-17; 2-19a; 2-22a; 2-25b; 2-29; 2-30; 2-31;

Thank you!

