



浙江大學
ZHEJIANG UNIVERSITY

Logic and Computer Design Fundamentals

Chapter 3 –Combinational Logic Design(1)


Ma De (马德)

made@zju.edu.cn

2023

College of Computer Science, Zhejiang University

Course Outline

 


Combinational Circuits

□ A combinational logic circuit has:

- A set of m Boolean inputs,
- A set of n Boolean outputs, and
- n switching functions, each mapping the 2^m input combinations to an output such that the current output depends only on the current input values

□ A block diagram:

 

m Boolean Inputs

n Boolean Outputs

Integrated Circuits

- ❑ Integrated circuit (informally, a “chip”) is a semiconductor crystal (most often silicon) containing the electronic components for the digital gates and storage elements which are interconnected on the chip.
- ❑ Terminology - Levels of chip integration
 - *SSI (small-scale integrated)* - fewer than 10 gates
 - *MSI (medium-scale integrated)* - 10 to 100 gates
 - *LSI (large-scale integrated)* - 100 to thousands of gates
 - *VLSI (very large-scale integrated)* - thousands to 100s of millions of gates

Technology Parameters

❑ Specific gate implementation technologies are characterized by the following parameters:

- *Fan-in* – the number of inputs available on a gate
- *Fan-out* – the number of standard loads driven by a gate output
- *Logic Levels* – the signal value ranges for 1 and 0 on the inputs and 1 and 0 on the outputs (see Figure 1-1)
- *Noise Margin* – the maximum external noise voltage superimposed on a normal input value that will not cause an undesirable change in the circuit output
- *Cost for a gate* - a measure of the contribution by the gate to the cost of the integrated circuit
- *Propagation Delay* – The time required for a change in the value of a signal to propagate from an input to an output
- *Power Dissipation* – the amount of power drawn from the power supply and consumed by the gate

Fan-out

□ Fan-out can be defined in terms of a standard load

- Example: 1 standard load equals the load contributed by the input of 1 inverter.
- *Transition time* -the time required for the gate output to change from H to L, t_{HL} , or from L to H, t_{LH}
- The *maximum fan-out* that can be driven by a gate is the number of standard loads the gate can drive without exceeding its specified *maximum transition time*

❑ In an integrated circuit:

- The cost of a gate is proportional to the chip area occupied by the gate
- The gate area is roughly proportional to the number and size of the transistors and the amount of wiring connecting them
- Ignoring the wiring area, the gate area is roughly proportional to the gate input count
- So gate input count is a rough measure of gate cost


❑ If the actual chip layout area occupied by the gate is known, it is a far more accurate measure



Propagation Delay

- ❑ *Propagation delay* is the time for a change on an input of a gate to propagate to the output.
- ❑ Delay is usually measured at the 50% point with respect to the H and L output voltage levels.
- ❑ High-to-low (t_{PHL}) and low-to-high (t_{PLH}) output signal changes may have different propagation delays.
- ❑ High-to-low (HL) and low-to-high (LH) transitions are defined with respect to the output, not the input.
- ❑ An HL input transition causes:
 - an LH output transition if the gate inverts and
 - an HL output transition if the gate does not invert.


Propagation Delay (continued)

 

- Propagation delays measured at the midpoint between the L and H values

Propagation Delay Example

 Find t_{PHL} , t_{PLH} and t_{pd} for the signals given






Delay Models

- ❑ *Transport delay* - a change in the output in response to a change on the inputs occurs after a fixed specified delay
- ❑ *Inertial delay* - similar to transport delay, except that if the input changes such that the output is to change twice in a time interval less than the *rejection time*, the output changes do not occur. Models typical electronic circuit behavior, namely, rejects narrow “pulses” on the outputs




Delay Model Example

 

Propagation Delay = 2.0 ns Rejection Time = 1.0 ns

Circuit Delay

   - Suppose gates with delay n ns are represented for $n = 0.2$ ns, $n = 0.4$ ns, $n = 0.5$ ns, respectively:





Circuit Delay

□ Consider a simple 2-input multiplexer:

□ With function:

  - $Y = A$ for $S = 0$
- $Y = B$ for $S = 1$



□ “Glitch” is due to delay of inverter

Fan-out and Delay

- ❑ The fan-out loading a gate's output affects the gate's propagation delay

- ❑ **Example:**

- One realistic equation for t_{pd} for a NAND gate with 4 inputs is:

$$t_{pd} = 0.07 + 0.021 \text{ SL ns}$$

- SL is the number of standard loads the gate is driving, i. e., its fan-out in standard loads
 - For $\text{SL} = 4.5$, $t_{pd} = 0.165 \text{ ns}$

- ❑ **If this effect is considered, the delay of a gate in a circuit takes on different values depending on the circuit load on its output.**

Cost/Performance Tradeoffs


□ Gate-Level Example:

- NAND gate G with 20 standard loads on its output has a delay of 0.45 ns and has a normalized cost of 2.0
- A buffer H has a normalized cost of 1.5. The NAND gate driving the buffer with 20 standard loads gives a total delay of 0.33 ns
- In which of the following cases should the buffer be added?
 1. The cost of this portion of the circuit cannot be more than 2.5
 2. The delay of this portion of the circuit cannot be more than 0.40 ns
 3. The delay of this portion of the circuit must be less than 0.40 ns and the cost less than 3.0

□ Tradeoffs can also be accomplished much higher in the design hierarchy

□ Constraints on cost and performance have a major role in making tradeoffs

Course Outline

 



Design Procedure

1. Specification

- Write a specification for the circuit if one is not already available

2. Formulation

- Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification
- Apply hierarchical design if appropriate

3. Optimization

- Apply 2-level and multiple-level optimization
- Draw a logic diagram or provide a netlist for the resulting circuit using ANDs, ORs, and inverters



Design Procedure

4. Technology Mapping

- Map the logic diagram or netlist to the implementation technology selected

5. Verification

- Verify the correctness of the final design manually or using simulation



Design Example

1. Specification

- BCD to Excess-3 code converter
- Transforms BCD code for the decimal digits to Excess-3 code for the decimal digits
- BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively
- Excess-3 code words for digits 0 through 9: 4-bit patterns consisting of 3 (binary 0011) added to each BCD code word
- Implementation:
 - multiple-level circuit
 - NAND gates (including inverters)

Design Example (continued)

2. Formulation

- Conversion of 4-bit codes can be most easily formulated by a truth table

- Variables
 - BCD:
 - A,B,C,D

- Variables
 - Excess-3
 - W,X,Y,Z

- Don't Cares
 - BCD 1010 to 1111

Input BCD A B C D	Output Excess-3 W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0

Design Example (continued)

3. Optimization (continued)

- b. Multiple-level using transformations

$$W = A + BC + BD$$

$$X = \overline{B}C + \overline{B}D + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

$$G = 7 + 10 + 6 + 0 = 23$$

- Perform extraction, finding factor:

$$T_1 = C + D$$

$$W = A + BT_1$$

$$X = \overline{B}T_1 + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

$$G = 2 + 4 + 7 + 6 + 0 = 19$$



Design Example (continued)

3. Optimization (continued)

- b. Multiple-level using transformations

$$T_1 = C + D$$

$$W = A + BT_1$$

$$X = \overline{B}T_1 + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

$$G = 19$$

- An additional extraction not shown in the text since it uses a Boolean transformation: ($\overline{C}\overline{D} = \overline{C + D} = \overline{T_1}$):

$$W = A + BT_1$$

$$X = \overline{B}T_1 + B\overline{T_1}$$

$$Y = CD + \overline{T_1}$$


$$Z = \overline{D}$$

$$G = 2 + 4 + 6 + 4 + 0 = 16!$$

Design Example (continued)

 4. Technology Mapping

- Mapping with a library containing inverters and 2-input NAND, 2-input NOR, and 2-2 AOI gates



Course Outline







Beginning Hierarchical Design

- ❑ To control the complexity of the function mapping inputs to outputs:
 - Decompose the function into smaller pieces called *blocks*
 - Decompose each block's function into smaller blocks, repeating as necessary until all blocks are small enough
 - Any block not decomposed is called a *primitive block*
 - The collection of all blocks including the decomposed ones is a *hierarchy*
- ❑ Example: (next slide)


Hierarchy for Parity Tree Example

 


(a) Symbol for circuit

 

 (b) Circuit as interconnected 3-input odd function blocks



 (c) 3-input odd function circuit as interconnected exclusive-OR blocks



(d) Exclusive-OR block as interconnected NANDs

➤ 9-input parity tree

- Top Level: 9 inputs, one output
- 2nd Level: Four 3-bit odd parity trees in two levels
- 3rd Level: Two 2-bit exclusive-OR functions
- Primitives: Four 2-input NAND gates
- Design requires $4 \times 2 \times 4 = 32$ 2-input NAND gates



Reusable Functions


- Whenever possible, we try to decompose a complex design into common, *reusable* function blocks
- These blocks are
 - verified and well-documented
 - placed in libraries for future use



Top-Down versus Bottom-Up

- ❑ A *top-down design* proceeds from an abstract, high-level specification to a more and more detailed design by decomposition and successive refinement
- ❑ A *bottom-up design* starts with detailed primitive blocks and combines them into larger and more complex functional blocks
- ❑ Design usually proceeds top-down to known building blocks ranging from complete CPUs to primitive logic gates or electronic components.
- ❑ Much of the material in this chapter is devoted to learning about combinational blocks used in top-down design.

Course Outline

 



Technology Mapping

□ Mapping Procedures

- To NAND gates
- To NOR gates
- Mapping to multiple types of logic blocks in covered in the reading supplement: Advanced Technology Mapping.



Mapping to NAND gates

□ Assumptions:


- Gate loading and delay are ignored
- Cell library contains an inverter and n -input NAND gates, $n = 2, 3, \dots$
- An AND, OR, inverter schematic for the circuit is available

□ The mapping is accomplished by:

- Replacing AND and OR symbols,
- Pushing inverters through circuit fan-out points, and
- Canceling inverter pairs


NAND Mapping Algorithm

1. Replace ANDs and ORs:

 


 2. Repeat the three steps of actions until there is at most one inverter between :


- A circuit input or driving NAND gate output, and
- The attached NAND gate inputs.




NAND Mapping Example

 


(a)

 

(b)

 

(c)

 

(d)

Mapping to NOR gates

□ Assumptions:


- Gate loading and delay are ignored
- Cell library contains an inverter and n -input NOR gates, $n = 2, 3, \dots$
- An AND, OR, inverter schematic for the circuit is available

□ The mapping is accomplished by:

- Replacing AND and OR symbols,
- Pushing inverters through circuit fan-out points, and
- Canceling inverter pairs


NOR Mapping Algorithm

1. Replace ANDs and ORs:

 


 2. Repeat the three steps of actions until there is at most one inverter between :

- A circuit input or driving NAND gate output, and
- The attached NAND gate inputs.




NOR Mapping Example

 



Course Outline

 



Verification

- ❑ **Verification - show that the final circuit designed implements the original specification**
- ❑ **Simple specifications are:**
 - truth tables
 - Boolean equations
 - HDL code
- ❑ **If the above result from formulation and are not the original specification, it is critical that the formulation process be flawless for the verification to be valid!**



Basic Verification Methods

□ Manual Logic Analysis

- Find the truth table or Boolean equations for the final circuit
- Compare the final circuit truth table with the specified truth table, or
- Show that the Boolean equations for the final circuit are equal to the specified Boolean equations

□ Simulation

- Simulate the final circuit (or its netlist, possibly written as an HDL) and the specified truth table, equations, or HDL description using test input values that fully validate correctness.
- The obvious test for a combinational circuit is application of all possible “care” input combinations from the specification

Verification Example: Manual Analysis



□ BCD-to-Excess 3 Code Converter

- Find the SOP Boolean equations from the final circuit.
- Find the truth table from these equations
- Compare to the formulation truth table

□ Finding the Boolean Equations:

$$T_1 = \overline{\overline{C + D}} = C + D$$

$$W = \overline{\overline{A} (\overline{T_1} \overline{B})} = A + B T_1$$

$$X = (T_1 B) (B \overline{C} \overline{D}) = \overline{B} T_1 + B \overline{C} \overline{D}$$

$$Y = \overline{C \overline{D}} + \overline{\overline{C} D} = CD + \overline{C} \overline{D}$$

Verification Example: Manual Analysis



- Find the circuit truth table from the equations and compare to specification truth table:

Input BCD A B C D	Output Excess-3 W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 0 1 1

The tables match!

Verification Example: Simulation




□ Simulation procedure:

- Use a schematic editor or text editor to enter a gate level representation of the final circuit
- Use a waveform editor or text editor to enter a test consisting of a sequence of input combinations to be applied to the circuit
 - This test should guarantee the correctness of the circuit if the simulated responses to it are correct
 - Short of applying all possible “care” input combinations, generation of such a test can be difficult

Verification Example: Simulation



 Enter BCD-to-Excess-3 Code Converter Circuit Schematic




-
- The timing diagram shows the waveforms for inputs A, B, C, and D. The horizontal axis represents time in nanoseconds (ns), with major ticks at 0, 50 ns, and 100 ns. The vertical axis is labeled 'INPUTS'.
- Input A:** A constant high signal from 0 ns to approximately 85 ns, then transitions to low until 100 ns, and returns to high.
 - Input B:** A constant low signal from 0 ns to 50 ns, then transitions to high until approximately 85 ns, and returns to low.
 - Input C:** A signal that is low from 0 ns to 25 ns, high from 25 ns to 50 ns, low from 50 ns to 75 ns, high from 75 ns to 85 ns, and low from 85 ns to 100 ns.
 - Input D:** A signal that is low from 0 ns to 15 ns, high from 15 ns to 30 ns, low from 30 ns to 40 ns, high from 40 ns to 50 ns, low from 50 ns to 60 ns, high from 60 ns to 70 ns, low from 70 ns to 80 ns, high from 80 ns to 85 ns, low from 85 ns to 100 ns.

- # Chapter 3- Part 1

Verification Example: Simulation



 □ Run the simulation of the circuit for 120 ns



□ Do the simulation output combinations match the original truth table?



Assignment

□ 3-7, 3-8, 3-11, 3-13, 3-14, 3-16, 3-27, 3-28, 3-29, 3-37, 3-44, 3-47, 3-50, 3-51, 3-52, 3-59